

Name of Student: _____

Enrollment No.: _____

Class: _____


Section: _____

Session: _____

Department of Electronics & Communication Engineering

Electronics Devices Lab Manual

Prepared By:
Dr. L N Gahalod

 

LAKSHMI NARAIN COLLEGE OF TECHNOLOGY

Kalchuri Nagar, Raisen Road, Bhopal (MP) - 462023

Vision & Mission of the Department

Vision

To be recognized as Center of Academic Excellence by imparting quality teaching and strengthening research and development activities with world class infrastructure in the field of Electronics and Communication Engineering.

Mission


- To establish a quality teaching learning process to provide application oriented, in-depth knowledge consistently.
- To establish state-of-the-art laboratories for academic excellence and to develop infrastructure through collaboration for quality research.
- To equip the students by blending theoretical knowledge and practical skills with employability and entrepreneurship traits for a bright successful career.
- To inculcate team spirit and leadership qualities to produce socially acceptable, eco-friendly and responsible citizens.

INDEX

Name of Student: _____ Enrollment No: _____

S. No.	Title of the Experiment	Date of Experiment	Date of Submission	Remark
1	To plot the V-I Characteristics of a P-N Junction diode, and calculate static and dynamic resistance.			
2	To plot the V-I characteristics of Zener Diode in reverse bias and to verify that Zener Diode acts as a Voltage Regulator.			
3	To plot the V-I characteristics of Light Emitting Diode (LED).			
4	To observe the output waveforms and determine ripple factor of a Half Wave Rectifier with and without filter.			
5	To observe the output waveforms and determine ripple factor of a Full Wave Rectifier with and without filter.			
6	To observe and draw the input and output characteristics of a transistor connected in Common Base (CB) configuration and calculate current gain, input and out resistance.			
7	To observe and draw the input and output characteristics of a transistor connected in Common Emitter (CE) configuration and calculate current gain, input and out resistance.			

8	To plot the frequency response of a Common Emitter Transistor Amplifier and determine the Bandwidth from the Response.			
9	To plot the Drain and Transfer characteristics of a given JFET and to calculate the Drain Resistance r_d , mutual Conductance g_m & Amplification factor μ .			
10	To plot the V-I Characteristics of Uni-Junction Transistor (UJT).			

 

Code of Conducts for the Laboratories

- All bags must be left at the indicated place.
- The lab timetable must be strictly followed.
- Be **PUNCTUAL** for your laboratory session.
- Noise must be kept to a minimum.
- Workspace must be kept clean and tidy at all time.
- Handle the experiment kit and interfacing kits with care.
- All students are liable for any damage to the accessories due to their own negligence.
- Students are strictly **PROHIBITED** from taking out any items from the laboratory.
- Students are **NOT** allowed to work alone in the laboratory without the Lab Supervisor
- Report immediately to the Lab Supervisor if any malfunction of the accessories, is there.
- Before leaving the lab Place the stools properly.
- Please check the laboratory notice board regularly for updates.

Date of Experiment _____

EXPERIMENT NO: 1

Aim: To plot the V-I Characteristics of a P-N Junction diode, and calculate static and dynamic resistance.

Apparatus Required:

1. P-N Diode IN4007 - 1No.
2. Regulated Power supply (0-30V) - 1No.
3. Resistor $1K\Omega$ - 1No.
4. Ammeter (0-20 mA) - 1No
5. Ammeter (0-200 μ A) - 1No.
6. Voltmeter (0-20V) - 2No.
7. Bread board
8. Connecting wires

Theory:

(A) Forward bias operation

The P-N junction supports uni-directional current flow. If +ve terminal of the input supply is connected to anode (P-side) and –ve terminal of the input supply is connected the cathode. Then diode is said to be forward biased. In this condition the height of the potential barrier at the junction is lowered by an amount equal to given forward biasing voltage. Both the holes from p-side and electrons from n-side cross the junction simultaneously and constitute a forward current from n-side cross the junction simultaneously and constitute a forward current (injected minority current – due to holes crossing the junction and entering P- side of the diode). Assuming current flowing through the diode to be very large, the diode can be approximated as short- circuited switch.

(B) Reverse bias operation

If negative terminal of the input supply is connected to anode (p-side) and –ve terminal of the input supply is connected to cathode (n-side) then the diode is said to be reverse biased. In this condition an amount equal to reverse biasing voltage increases the height of the potential barrier at the junction.

Both the holes on P-side and electrons on N-side tend to move away from the junction there by increasing the depleted region. However the process cannot continue indefinitely, thus a small current called reverse saturation current continues to flow in the diode. This current is negligible; the diode can be approximated as an open circuited switch.

Diode current equation

The volt-ampere characteristics of a diode explained by the following equations:

$$I = I_0 \left(e^{V/\eta V_T} - 1 \right)$$

where

I = current flowing in the diode, I_0 = reverse saturation current

V = Voltage applied to the diode

V_T = volt- equivalent of temperature = $k T/q = T/ 11,600 = 26\text{mV}$


$\eta = 1$ (for Ge) and 2 (for Si)

It is observed that Ge diodes has smaller cut-in-voltage when compared to Si diode. The reverse saturation current in Ge diode is larger in magnitude when compared to silicon diode.

Circuit Diagram:

(A) Forward bias operation

Figure 1:
Forward
Bias
Operation

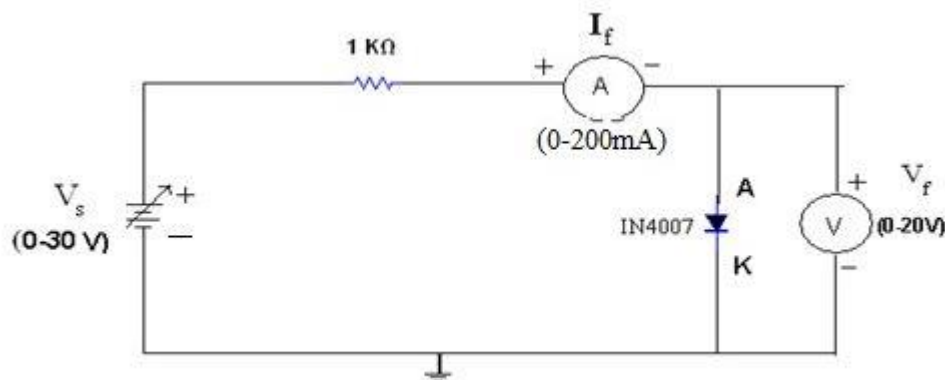

(B) Reverse bias operation

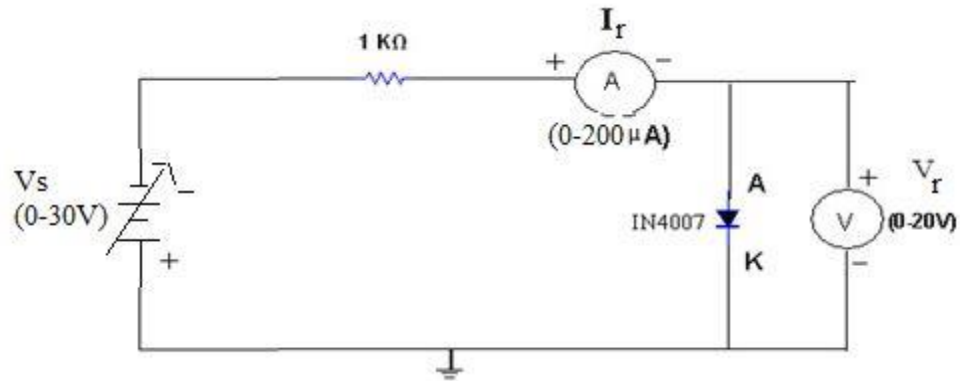


Figure 2: Reverse Bias Operation

Procedure:

Forward Bias Operation

- 1) Connect the circuit as shown in figure (1) using PN Junction diode.
- 2) Initially vary Regulated Power Supply (RPS) voltage V_s in steps of **0.2 V**.
- 3) Once the current starts increasing vary V_s from **1V** to **10V** in steps of **1V** and note down the corresponding readings V_f and I_f .
- 4) Tabulate different forward currents obtained for different forward voltages.

Reverse Bias Operation

- 1) Connect the circuit as shown in figure (2) using PN Junction diode.
- 2) Vary V_s in the Regulated Power Supply (RPS) gradually in steps of **1V** from **0V** to **10V** and note down the corresponding readings V_r and I_r .
- 3) Tabulate different reverse currents obtained for different reverse voltages.

Observations:


Forward Bias Operation:

Input Voltage (V_{in})	Forward Voltage (V_f)	Forward Current (I_f)
0.0		
0.2		
0.4		
0.6		
0.8		
1.0		
2.0		
3.0		
4.0		
5.0		
6.0		
7.0		
8.0		
9.0		
10.0		

Reverse Bias Operation:

Input Voltage (V_{in})	Reverse Voltage (V_r)	Reverse Current (I_r)
1.0		
2.0		
3.0		
4.0		
5.0		
6.0		
7.0		
8.0		
9.0		
10.0		

Plot the graph on the graph paper

 

Calculations from Graph:

Static forward Resistance $R_{dc} = \frac{V_f}{I_f} \Omega$

Dynamic Forward Resistance $r_{ac} = \frac{\Delta V_f}{\Delta I_f} \Omega$

Result: Volt-Ampere Characteristics of P-N Diode are studied.

The Cut in Voltage or Knee Voltage (V_γ) of 1N4007 _____ Volts.

The Dynamic Forward resistance of 1N4007 is _____ Ω .

The Static Forward resistance of 1N4007 is _____ Ω .

Signature of Faculty

Date of Experiment _____

EXPERIMENT NO: 2

Aim: To plot the V-I characteristics of Zener Diode in reverse bias and to verify that Zener Diode acts as a Voltage Regulator.

Apparatus Required:

1. Zener diode IMZ5.1 V.
2. 470Ω resistor.
3. Ammeter (0-50mA).
4. Voltmeter (0-10V).
5. RPS (0-30V).
6. Bread Board.
7. Decade Resistance Box (DRB).
8. Connecting Wires.

Theory: A Zener diode is heavily doped p-n junction diode, specially made to operate in the break down region. A p-n junction diode normally does not conduct when reverse biased. But if the reverse bias is increased, at a particular voltage it starts conducting heavily. This voltage is called Break down Voltage. High current through the diode can permanently damage the device.


To avoid high current, we connect a resistor in series with Zener diode. Once the diode starts conducting it maintains almost constant voltage across the terminals whatever may be the current through it, i.e., it has very low dynamic resistance. It is used in voltage regulators.

V-I Characteristics

Procedure: 1. Make the connections as shown in the circuit diagram.

2. Vary the RPS voltage from 0V to 30V in steps of 1V.
3. Tabulate the readings of Ammeter (I_Z) and Voltmeter (V_Z).
4. Plot the graph between V_Z & I_Z .
5. Calculate the break down voltage of given Zener diode from the graph

Circuit Diagram:

 

Observation Table:

Sr. No	V_s (volts)	V_z (volts)	I_z (volts)
1	1 V		
2	2 V		
3	3 V		
4	4 V		
5	5 V		
6	6 V		
7	7 V		
8	8 V		
9	9 V		
10	10 V		

Voltage Regulator:

Procedure: 1. Make the connections as shown in figure 2.


2. Measure V_{NL} (No load voltage) by opening the load resistance.

3. Connect the load resistance, and vary the load resistance from 1000Ω to 100Ω in steps of 100Ω and note down the readings of Voltmeter (V_Z) and Ammeter (I_S).

1. Calculate % Regulation by using the formula given below.

$$\% \text{ Regulation} = \frac{V_{NL} - V_L}{V_{NL}} \times 100\%$$

Circuit Diagram:

 


Observation Table:

$V_{NL} = \underline{\hspace{2cm}}$ volts

Sr. No.	R_L (ohms)	V_L (volts)	$I_S (I_Z + I_L)$ (mA)	% Regulation
1	1000			
2	900			
3	800			
4	700			
5	600			
6	500			
7	400			
8	300			
9	200			
10	100			

Plot the graph on graph paper

 

Result:

1. The Zener breakdown voltage = _____ volts
2. The reverse bias characteristics of Zener diode are observed and plotted on the graph.
3. The Regulation characteristics of a Zener Diode are observed and plotted on the graph.

Signature of Faculty

Date of Experiment _____

EXPERIMENT NO: 3

Aim: To plot the V-I characteristics of Light Emitting Diode (LED).


Apparatus Required: 1. L.E.D

2. 470Ω resistor
3. Ammeter (0-100ma)
4. Voltmeter (0-20v)
5. RPS
6. Bread board
7. Connecting wires

Theory: The “**Light Emitting Diode**” or LED as it is more commonly called, is basically just a specialised type of diode as they have very similar electrical characteristics to a PN junction diode. This means that an LED will pass current in its forward direction but block the flow of current in the reverse direction.

Light Emitting Diodes are made from exotic semiconductor compounds such as Gallium Arsenide (GaAs), Gallium Phosphide (GaP), Gallium Arsenide Phosphide (GaAsP), Silicon Carbide (SiC) or Gallium Indium Nitride (GaInN) all mixed together at different ratios to produce a distinct wavelength of colour.

Circuit Diagram:

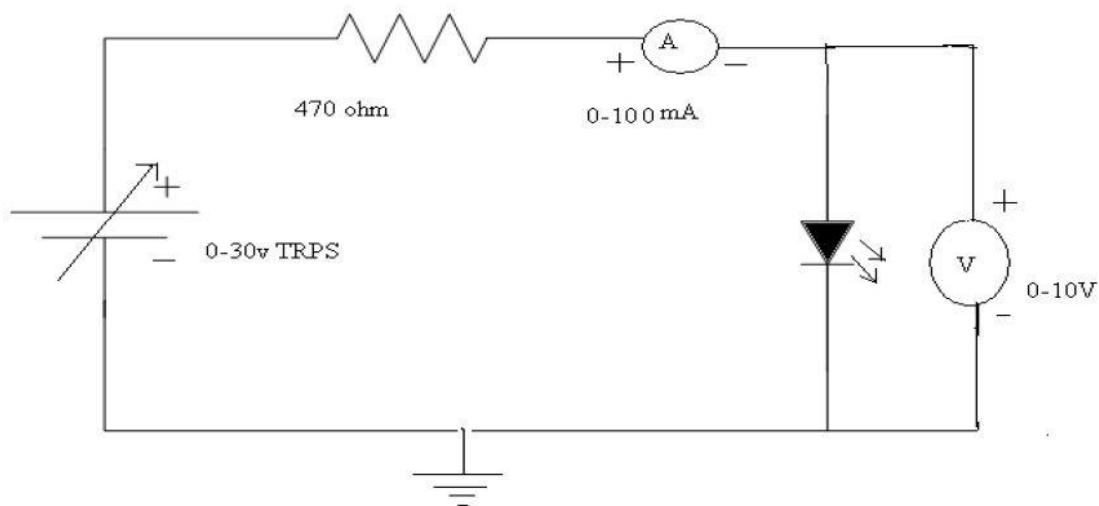

Procedure:


1. Connections must be made as per the circuit diagram.
2. By varying the voltage in steps corresponding current in the ammeter is noted.
3. At the same time the glow intensity of the light emitting diode is also to be noted.
4. Taking voltage on X-axis and current on Y-axis that gives the forward bias V-I characteristics, plot a graph.

Observation Table:

Sr. No.	V_s (volts)	V_f (volts)	I_f (volts)	Intensity of glow
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				

Result: The forward characteristics of a light emitting diode are obtained and plotted in graph paper.

Signature of Faculty

 

Signature of Faculty

Date of Experiment _____

EXPERIMENT NO: 4

Aim: To observe the output waveforms and determine ripple factor of a Half Wave Rectifier with and without filter.

Apparatus Required: 1. 230-12V Step down Transformer – 1no.

2. IN 4007 Diode – 1no.

3. 0-20V Voltmeter /DMM – 1no.

4. 0-100mA Millimeter/DMM – 1no.

5. 1K Ω , 2K Ω , 10K Ω resistor – 1each.

6. 100 μ f/25V capacitor – 1no.

7. Bread Board.

8. Connecting wires.

Theory: In Half Wave Rectification, When AC supply is applied at the input, only Positive Half Cycle appears across the load whereas, the negative Half Cycle is suppressed. How this can be explained as follows:

During positive half-cycle of the input voltage, the diode D_1 is in forward bias and conducts through the load resistor R_L . Hence the current produces an output voltage across the load resistor R_L , which has the same shape as the +ve half cycle of the input voltage.

During the negative half-cycle of the input voltage, the diode is reverse biased and there is no current through the circuit. i.e., the voltage across R_L is zero. The net result is that only the +ve half cycle of the input voltage appears across the load. The average value of the half wave rectified o/p voltage is the value measured on dc voltmeter.

Theoretical calculations for Ripple factor:

Without Filter:

$$V_{rms} = \frac{V_m}{2} \text{ or } V_m = 2V_{rms}$$

$$V_{dc} = \frac{V_m}{\pi}$$

$$\text{Ripple factor} = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

With Filter:

$$\text{Ripple factor} = \frac{1}{2\sqrt{3}fR_LC}$$

Circuit Diagram:

Half Wave Rectifier without Filter:

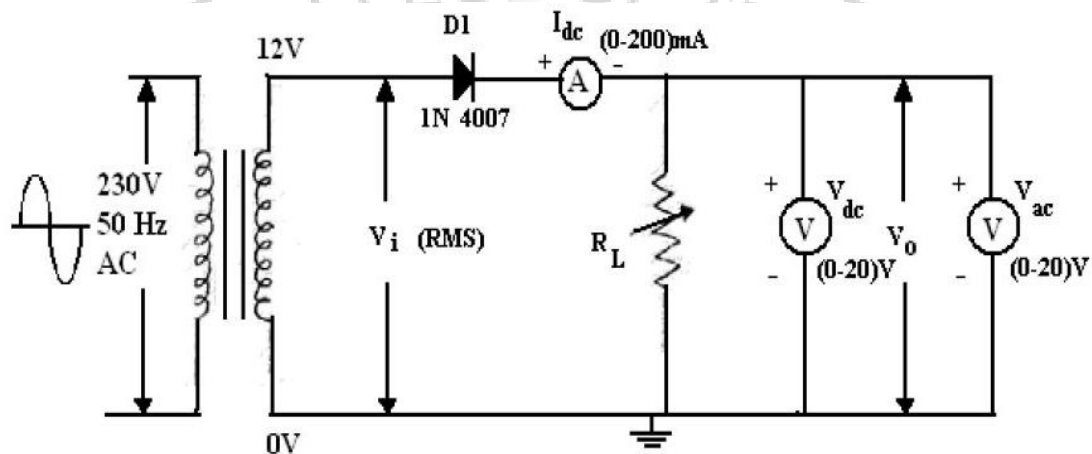


Figure a: Half Wave Rectifier without filter

Half Wave Rectifier with Filter

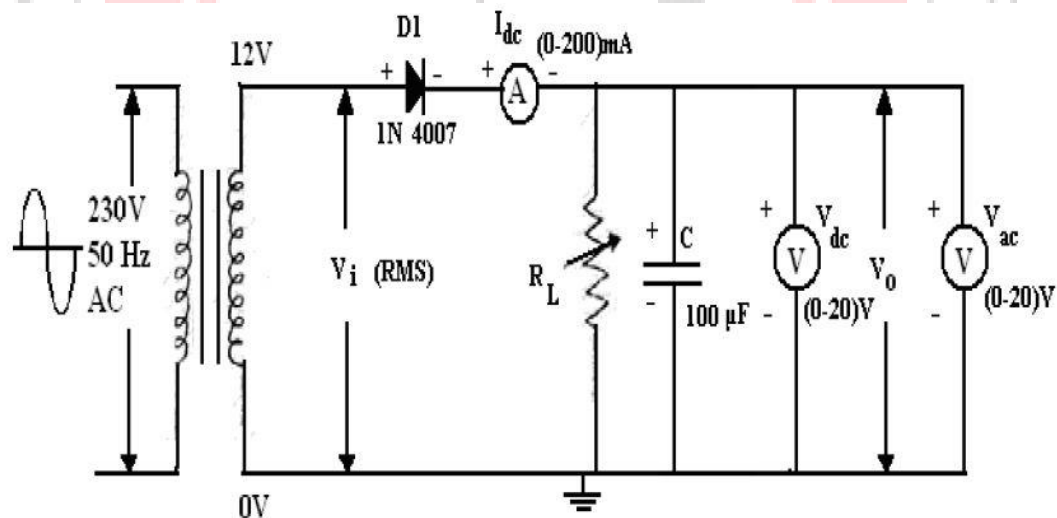


Figure b: Half Wave Rectifier with filter

Procedure:

1. Connect the circuit as shown in figure (a).

2. Adjust the load resistance, R_L to 500Ω , and note down the readings of input and output voltages through oscilloscope.
3. Note the readings of dc current, dc voltage and ac voltage.
4. Now, change the resistance the load resistance, R_L to $1\text{ K}\Omega$ and repeat the procedure as above. Also repeat for $10\text{ K}\Omega$.
5. Readings are tabulated as per the tabular column.
6. Connect the circuit as shown in figure (b) and repeat the procedure.

Observation Table:

Half Wave Rectifier without Filter

Sr. No.	R_L (ohms)	Average DC current (I_{dc})	Average DC voltage (V_{dc})	RMS voltage (V_{ac})	Ripple factor (V_{ac}/V_{dc})
1	1K				
2	2K				
3	10K				

Half Wave Rectifier with Filter with $C = 100\mu\text{F}$

Sr. No.	R_L (ohms)	Average DC current (I_{dc})	Average DC voltage (V_{dc})	RMS voltage (V_{ac})	Ripple factor (V_{ac}/V_{dc})
1	1K				
2	2K				
3	10K				

Result:

1. Input and Output waveforms of a half-wave with /without filter are observed and plotted.

2. For Half-wave rectifier without filter:-


Ripple factor at $1\text{ K}\Omega = \underline{\hspace{1cm}}$, $2\text{ K}\Omega = \underline{\hspace{1cm}}$, $10\text{ K}\Omega = \underline{\hspace{1cm}}$.

3. For Half-wave rectifier with filter:-

Ripple factor at $1\text{K}\Omega$, $100\mu\text{F}$ =

$2\text{K}\Omega$, $100\mu\text{F}$ =

$10\text{K}\Omega$, $100\mu\text{F}$ =

 

Signature of Faculty

Date of Experiment _____

EXPERIMENT NO: 5

Aim: To observe the output waveforms and determine ripple factor of a Full Wave Rectifier with and without filter.

Apparatus Required: 1. 230-12V Centre tapped Step down Transformer

2. IN 4007 Diode – 2no.
3. 0-20V Voltmeter /DMM – 1no.
4. 0-100mA Millimeter/DMM – 1no.
5. 1K Ω , 2K Ω , 10K Ω resistor – 1each.
6. 100 μ f/25V capacitor – 1no.
7. Bread Board.
8. Connecting wires.

Theory: The circuit of a center-tapped full wave rectifier uses two diodes D₁ & D₂. During positive half cycle of secondary voltage (input voltage), the diode D₁ is forward biased and D₂ is reverse biased.

The diode D₁ conducts and current flows through load resistor R_L. During negative half cycle, diode D₂ becomes forward biased and D₁ reverse biased. Now, D₂ conducts and current flows through the load resistor R_L in the same direction. There is a continuous current flow through the load resistor R_L, during both the half cycles and will get unidirectional current as show in the model graph. The difference between full wave and half wave rectification is that a full wave rectifier allows unidirectional (one way) current to the load during the entire 360 degrees of the input signal and half-wave rectifier allows this only during one half cycle (180 degree).

Theoretical calculations for Ripple factor:

Without Filter:

$$V_{rms} = \frac{V_m}{\sqrt{2}} \text{ or } V_m = \sqrt{2}V_{rms}$$

$$V_{dc} = \frac{2V_m}{\pi}$$


$$\text{Ripple factor} = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

With Filter:


$$\text{Ripple factor} = \frac{1}{2\sqrt{3}fR_LC}$$

Circuit Diagram:

Full Wave Rectifier without Filter:

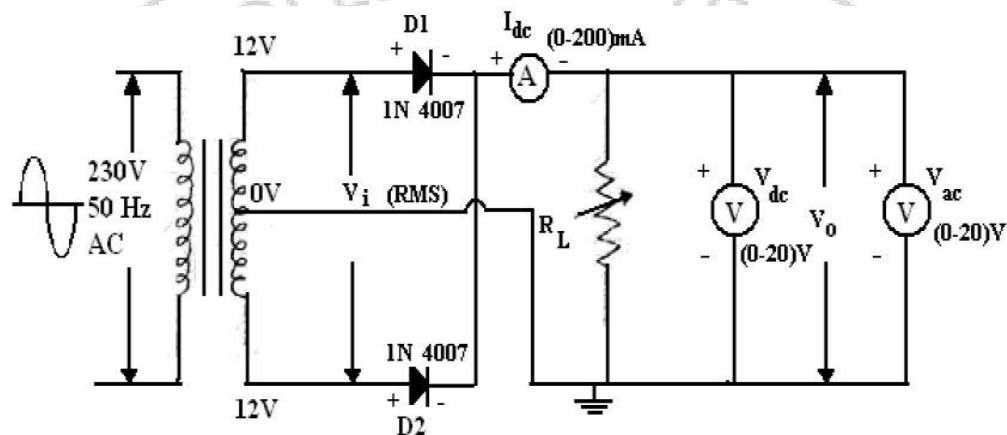

Full Wave Rectifier with Filter:

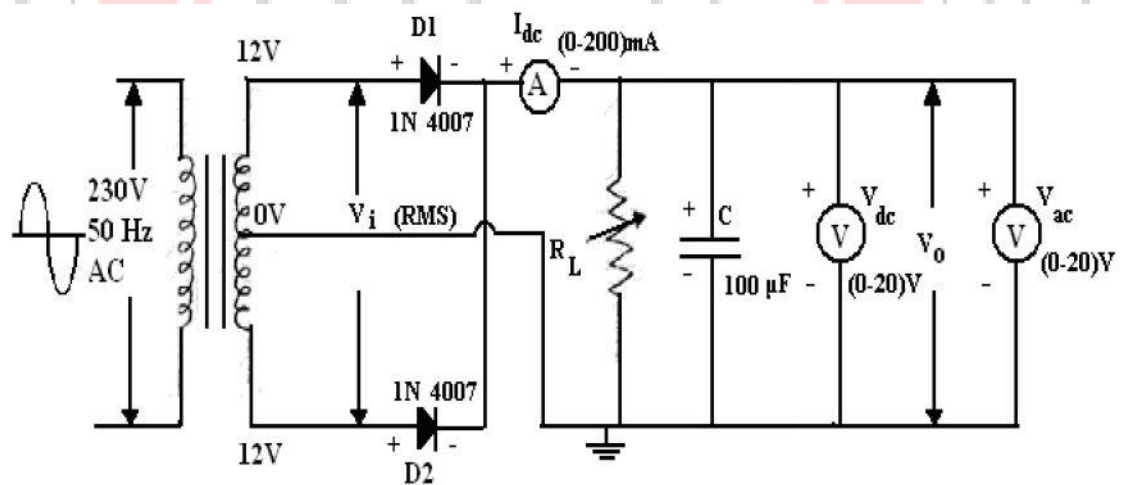

Procedure:

1. Connect the circuit as shown in the figure (a).
2. Adjust the load resistance R_L to $1K\Omega$ and note the readings of input and output voltages through Oscilloscope.

3. Note the readings of DC current, DC voltage and AC voltage.
4. Now change the load resistance R_L to $2K\Omega$ and repeat the procedure as the above.
5. Readings are tabulate as per the tabular column.
6. Connect a capacitor of $100\mu F$ values in parallel with the load and repeat the above procedure.

Observation Table:

Full Wave Rectifier without Filter

Sr. No.	R_L (ohms)	Average DC current (I_{dc})	Average DC voltage (V_{dc})	RMS voltage (V_{ac})	Ripple factor (V_{ac}/V_{dc})
1	1K				
2	2K				
3	10K				

Full Wave Rectifier with Filter with $C = 100\mu F$

Sr. No.	R_L (ohms)	Average DC current (I_{dc})	Average DC voltage (V_{dc})	RMS voltage (V_{ac})	Ripple factor (V_{ac}/V_{dc})
1	1K				
2	2K				
3	10K				


Result:

1. Input and Output waveforms of a Full-wave with /without filter are observed and plotted.
2. For Full-wave rectifier without filter:-
Ripple factor at $1K\Omega = \underline{\hspace{1cm}}$, $2K\Omega = \underline{\hspace{1cm}}$, $10 K\Omega = \underline{\hspace{1cm}}$.
3. For Full-wave rectifier with filter:-

Ripple factor at $1\text{K}\Omega, 100\mu\text{F} =$

$2\text{K}\Omega, 100\mu\text{F} =$

$10\text{K}\Omega, 100\mu\text{F} =$

 

Signature of Faculty

Date of Experiment _____

EXPERIMENT NO: 6

Aim: To observe and draw the input and output characteristics of a transistor connected in Common Base (CB) configuration and calculate current gain, input and out resistance.

Apparatus Required:

1. Transistor, BC107 -1No.
2. Regulated power supply (0-30V) -2No.
3. Voltmeter (0-20V) - 2No.
4. Ammeters (0-20mA) - 2No.
5. Resistor, $1K\Omega$ - 2No
6. Bread Board.
7. Connecting wires.

Theory: A transistor is a three terminal active device. The terminals are emitter, base, collector. In CB configuration, the base is common to both input (emitter) and output (collector). For normal operation, the E-B junction is forward biased and C-B junction is reverse biased.

With an increasing the reverse collector voltage, the space-charge width at the output junction increases and the effective base width 'W' decreases. This phenomenon is known as "Early effect". Then, there will be less chance for recombination within the base region. With increase of charge gradient with in the base region, the current of minority carriers injected across the emitter junction increases.


The current amplification factor of CB configuration is given by,

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$\text{Input Resistance } R_i = \frac{\Delta V_{BE}}{\Delta I_E} \text{ at constant } V_{CB}$$

$$\text{Output Resistance } R_o = \frac{\Delta V_{CB}}{\Delta I_C} \text{ at constant } I_E$$

Circuit Diagram:

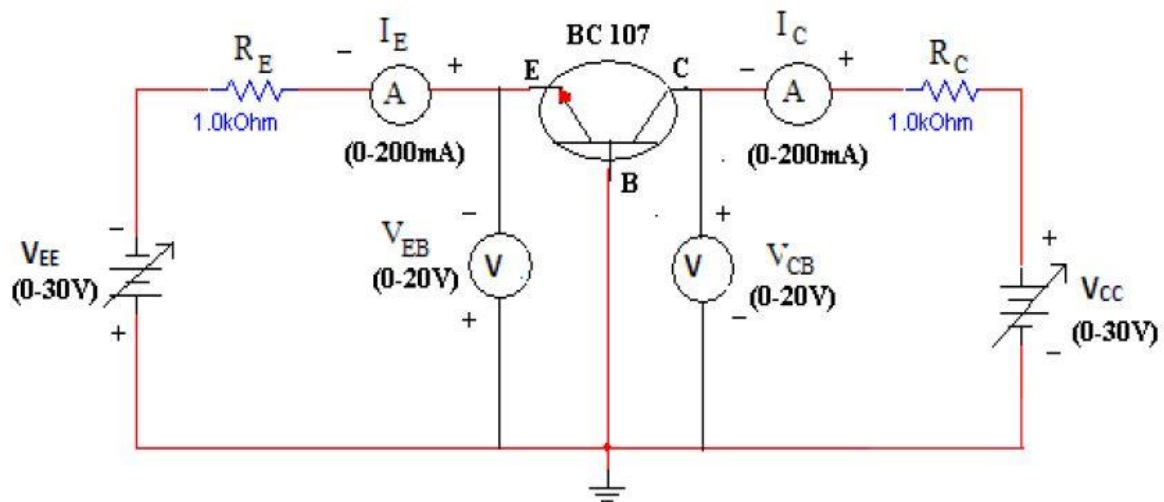

Procedure:

Input Characteristics:

1. Connections are made as per the circuit diagram.
2. For plotting the input characteristics, the output voltage V_{CE} is kept constant at 0V and for different values of V_{EE} note down the values of I_E and V_{BE} .
3. Repeat the above step keeping V_{CB} at 2V, 4V, and 6V and all the readings are tabulated.
4. A graph is drawn between V_{BE} and I_E for constant V_{CB} .

Output Characteristics:

1. Connections are made as per the circuit diagram.
2. For plotting the output characteristics, the input I_E is kept constant at 0.5mA and for different values of V_{CC} , note down the values of I_C and V_{CB} .
3. Repeat the above step for the values of I_E at 1mA, 5mA and all the readings are tabulated.
4. A graph is drawn between V_{CB} and I_C for constant I_E .

Observation:


Input Characteristics:

Sr. No.	$V_{CB} =$		$V_{CB} =$		$V_{CB} =$	
	$V_{EB} (V)$	$I_E (mA)$	$V_{EB} (V)$	$I_E (mA)$	$V_{EB} (V)$	$I_E (mA)$
1						
2						
3						
4						
5						
6						
7						
8						
9						
10						

Output Characteristics:

Sr. No.	$I_E =$		$I_E =$		$I_E =$	
	$V_{CB} (V)$	$I_C (mA)$	$V_{CB} (V)$	$I_C (mA)$	$V_{CB} (V)$	$I_C (mA)$
1						
2						
3						
4						
5						
6						
7						
8						
9						
10						

Graph is plotted on graph paper

 

Result: The input and output characteristics of transistor in CB configuration is observed and the plotted on graph paper.

Current gain $\alpha = \underline{\hspace{2cm}}$

Input Resistance $R_i = \underline{\hspace{2cm}}$ ohm.

Output Resistance $R_o = \underline{\hspace{2cm}}$ ohm

Signature of Faculty

Date of Experiment _____

EXPERIMENT NO: 7

Aim: To observe and draw the input and output characteristics of a transistor connected in Common Emitter (CE) configuration and calculate current gain, input and out resistance.

Apparatus Required: 1. Transistor, BC107 -1No.

2. Regulated power supply (0-30V) -2No.

3. Voltmeter (0-20V) - 2No.

4. Ammeters (0-20mA) - 1No.

5. Ammeters (0-200 μ A) - 1No.

6. Resistor, 100 Ω , 1K Ω – 1 each

7. Bread Board.

8. Connecting wires.

Theory: In common emitter configuration, input voltage is applied between base and emitter terminals and output is taken across the collector and emitter terminals. Therefore the emitter terminal is common to both input and output.

The input characteristics resemble that of a forward biased diode curve. This is expected since the Base-Emitter junction of the transistor is forward biased. As compared to CB arrangement I_B increases less rapidly with V_{BE} . Therefore input resistance of CE circuit is higher than that of CB circuit.


The output characteristics are drawn between I_C and V_{CE} at constant I_B the collector current varies with V_{CE} up to few volts only. After this the collector current becomes almost constant, and independent of V_{CE} . The value of V_{CE} up to which the collector current changes with V_{CE} is known as Knee voltage. The transistor always operated in the region above Knee voltage, I_C is always constant and is approximately equal to I_B . The current amplification factor of CE configuration is given by

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

Input Resistance $R_i = \frac{\Delta V_{BE}}{\Delta I_B}$ at constant V_{CE}

Output Resistance $R_o = \frac{\Delta V_{CE}}{\Delta I_C}$ at constant I_B

Circuit Diagram:

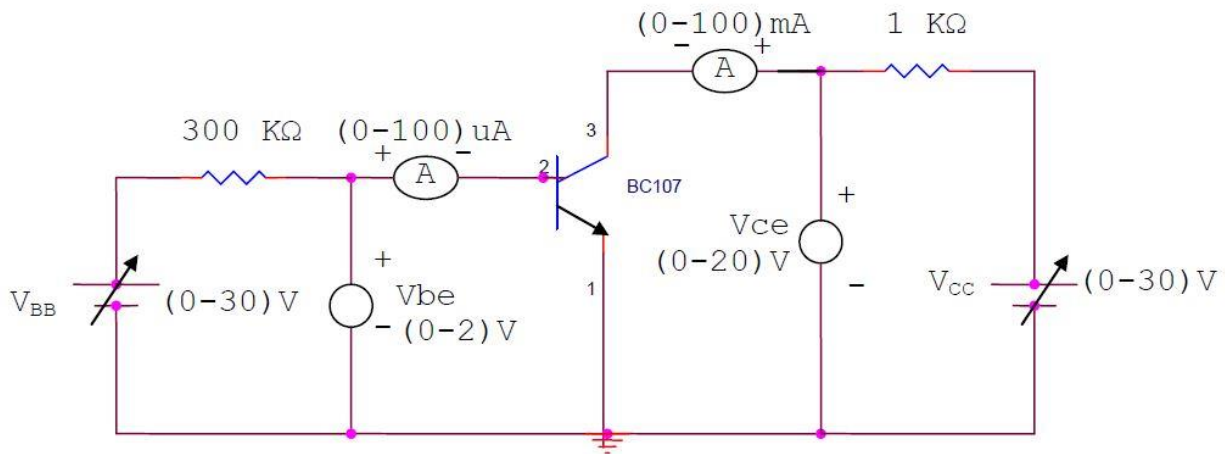

Procedure:

Input Characteristics:

1. Connect the circuit as per the circuit diagram.
2. For plotting the input characteristics the output voltage V_{CE} is kept constant at 1V and for different values of V_{BB} , note down the values of I_B and V_{BE}
3. Repeat the above step by keeping V_{CE} at 2V and 4V and tabulate all the readings.
4. Plot the graph between V_{BE} and I_B for constant V_{CE} .

Output Characteristics:

1. Connect the circuit as per the circuit diagram
2. For plotting the output characteristics the input current I_B is kept constant at $50\mu A$ and for different values of V_{CC} note down the values of I_C and V_{CE}
3. Repeat the above step by keeping I_B at $75\mu A$ and $100\mu A$ and tabulate the all the readings
4. Plot the graph between V_{CE} and I_C for constant I_B .

Observation:


Input Characteristics:

Sr. No.	$V_{CE} =$		$V_{CE} =$		$V_{CE} =$	
	V_{BE} (V)	$I_B(\mu A)$	V_{BE} (V)	$I_B(\mu A)$	V_{BE} (V)	$I_B(\mu A)$
1						
2						
3						
4						
5						
6						
7						
8						
9						
10						

Output Characteristics:

Sr. No.	$I_B =$		$I_B =$		$I_B =$	
	V_{CE} (V)	$I_C(mA)$	V_{CE} (V)	$I_C(mA)$	V_{CE} (V)	$I_C(mA)$
1						
2						
3						
4						
5						
6						
7						
8						
9						
10						

Graph is plotted on graph paper

 

Result: The input and output characteristics of transistor in CE configuration is observed and the plotted on graph paper.

Current gain $\beta = \underline{\hspace{2cm}}$

Input Resistance $R_i = \underline{\hspace{2cm}}$ ohm

Output Resistance $R_o = \underline{\hspace{2cm}}$ ohm

Signature of Faculty

Date of Experiment _____

EXPERIMENT NO: 8

Aim: To plot the frequency response of a Common Emitter Transistor Amplifier and determine the Bandwidth from the Response.

Apparatus Required: 1. Transistor BC107 -1No.

2. Regulated power Supply (0-30V) -1No.

3. Function Generator -1No.

4. CRO -1No.

5. Resistors [1K (2), 4.7K (1), 10K (2), 100K (1)]


6. Capacitors, 10 μ F -3No.

7. Bread Board

8. Connecting wires.

Theory: The CE amplifier provides high gain & wide frequency response. The emitter lead is common to both input & output circuits and is grounded. The emitter-base circuit is forward biased. The collector current is controlled by the base current rather than emitter current. When a transistor is biased in active region it acts like an amplifier. The input signal is applied to base terminal of the transistor and amplifier output is taken across collector terminal. A very small change in base current produces a much larger change in collector current. When positive half-cycle is fed to the input circuit, it opposes the forward bias of the circuit which causes the collector current to decrease; it decreases the voltage more negative. Thus when input cycle varies through a negative half-cycle, increases the forward bias of the circuit, which causes the collector current to increase thus the output signal is common emitter amplifier is in out of phase with the input signal. An amplified output signal is obtained when this fluctuating collector current flows through a collector resistor R_C .

The capacitor across the collector resistor R_C will act as a bypass capacitor. This will improve high frequency response of amplifier.

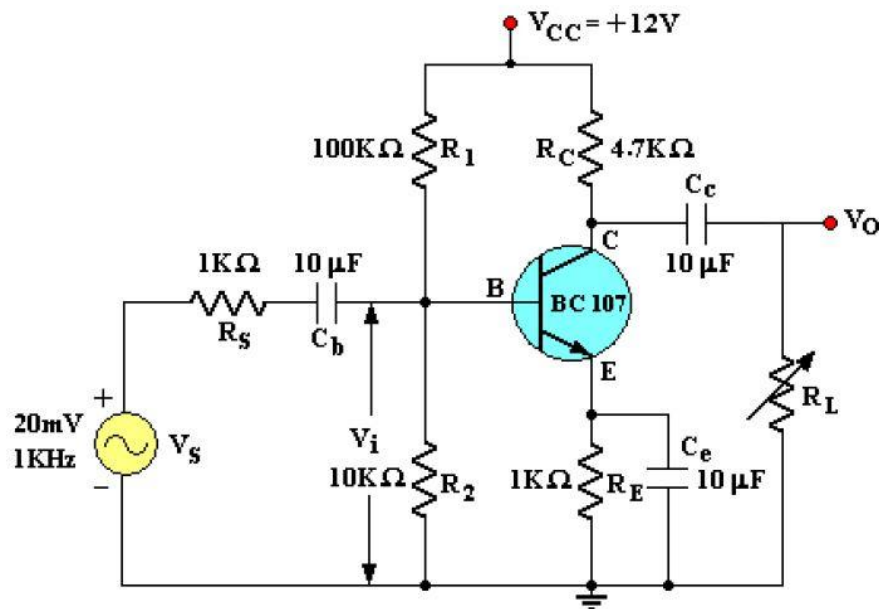Circuit Diagram:**Procedure:**

1. Connect the circuit as shown in figure, apply V_{CC} of 12 Volts DC.
2. Apply I/P Voltage of 20mV at 1KHz from the Signal Generator and observe the O/P on CRO.
3. Vary the frequency from 100 Hz to 1MHz in appropriate steps and note down the corresponding O/P Voltage V_o in a tabular form.
4. Calculate the Voltage Gain $A_v = V_o/V_s$ and note down in the tabular form.
5. Plot the frequency (f) V/s Gain (A_v) on a Semi-log Graph paper.
6. Mark the lower cutoff frequency (f_L) and higher cutoff frequency (f_H) at 70.7% of maximum gain point. And calculate the Bandwidth $BW = f_H - f_L$.

Observation:

Signal Voltage $V_s = \underline{\hspace{2cm}}$ volts

Sr. No.	Signal Frequency (Hz)	Output Voltage V_o (volts)	Gain $A_v = V_o/V_s$	decibel Gain $20\log(A_v)$ dB
1	100 Hz			
2	200 Hz			
3	500 Hz			
4	1K Hz			
5	2K Hz			
6	5K Hz			
7	10K Hz			
8	20K Hz			
9	50K Hz			
10	100K Hz			
11	200K Hz			
12	500K Hz			
13	1M Hz			


Result:

Lower cutoff frequency (f_L) = Hz

Higher cutoff frequency (f_H) = Hz

Bandwidth (BW) = Hz

Graph is plotted on graph paper

 

Signature of Faculty

Date of Experiment _____

EXPERIMENT NO: 9

Aim: To plot the Drain and Transfer characteristics of a given JFET and to calculate the Drain Resistance r_d , mutual Conductance g_m & Amplification factor μ .

Apparatus Required: 1. RPS (0-30v) - 2no.

2. Voltmeters (0-2)V & (0-20)V

3. JFET BFW10

4. Resistance 1K

5. Connecting wires

6. Bread board

Theory: A FET is a three terminal device, in which current conduction is by majority carriers only. The flow of current is controlled by means of an Electric field. The three terminals of FET are Gate, Drain and Source. It is having the characteristics of high input impedance and less noise, the Gate to Source junction of the FETs always reverse biased. In response to small applied voltage from drain to source, the n-type bar acts as sample resistor, and the drain current increases linearly with V_{DS} . With increase in I_D the ohmic voltage drop between the source and the channel region reverse biases the junction and the conducting position of the channel begins to remain constant. The V_{DS} at this instant is called “pinch of voltage”. If the gate to source voltage (V_{GS}) is applied in the direction to provide additional reverse bias, the pinch off voltage will be decreased. In amplifier application, the FET is always used in the region beyond the pinch-off.

FET parameters:

$$\text{AC Drain Resistance } r_d = \frac{\Delta V_{DS}}{\Delta I_D} \text{ at constant } V_{GS}$$

$$\text{Transconductance } g_m = \frac{\Delta I_D}{\Delta V_{GS}} \text{ at constant } V_{DS}$$

$$\text{Amplification factor } \mu = \frac{\Delta V_{DS}}{\Delta V_{GS}} \text{ at constant } I_D$$


The relation between above parameters is given by

$$\mu = r_d \times g_m$$

The drain current is given by

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

Circuit Diagram:

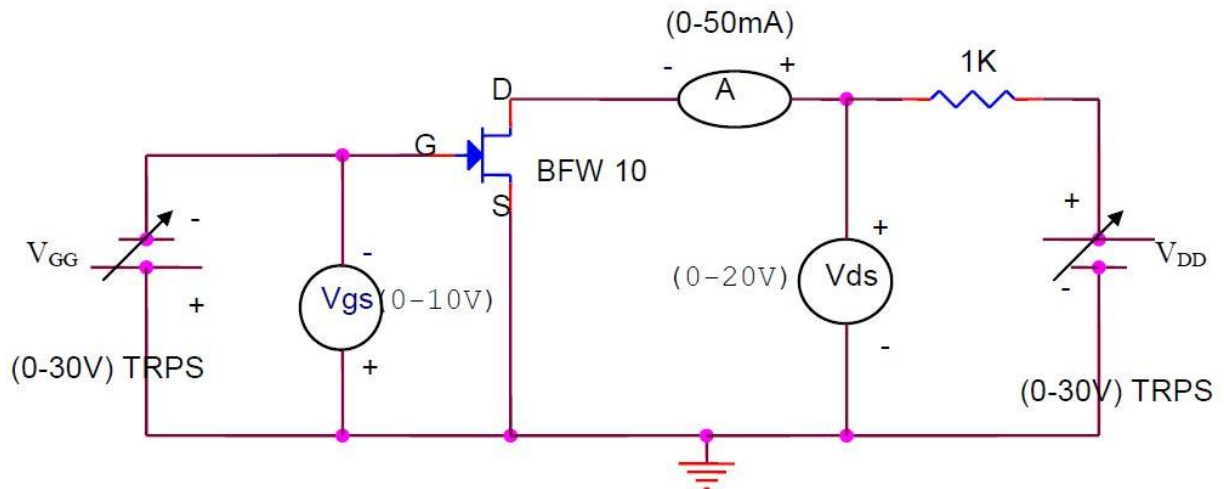

Procedure:

1. All the connections are made as per the circuit diagram.
2. To plot the drain characteristics, keep V_{GS} constant at 0V.
3. Vary the V_{DD} and observe the values of V_{DS} and I_D .
4. Repeat the above steps 2, 3 for different values of V_{GS} at 0.1V and 0.2V.
5. All the readings are tabulated.
6. To plot the transfer characteristics, keep V_{DS} constant at 1V.
7. Vary V_{GG} and observe the values of V_{GS} and I_D .
8. Repeat steps 6 and 7 for different values of V_{DS} at 1.5 V and 2V.
9. The readings are tabulated.
10. From drain characteristics, calculate the values of dynamic resistance (r_d)
11. From transfer characteristics, calculate the value of trans-conductance (g_m)

12. And also calculate Amplification factor (μ).

Observation:


Drain Characteristics

Sr. No.	$V_{GS} = \underline{\hspace{1cm}}$ volts		$V_{GS} = \underline{\hspace{1cm}}$ volts		$V_{GS} = \underline{\hspace{1cm}}$ volts	
	V_{DS} (V)	I_D (mA)	V_{DS} (V)	I_D (mA)	V_{DS} (V)	I_D (mA)
1						
2						
3						
4						
5						
6						
7						
8						

Transfer Characteristics:

Sr. No.	$V_{DS} = \underline{\hspace{1cm}}$ volts		$V_{DS} = \underline{\hspace{1cm}}$ volts		$V_{DS} = \underline{\hspace{1cm}}$ volts	
	V_{GS} (V)	I_D (mA)	V_{GS} (V)	I_D (mA)	V_{GS} (V)	I_D (mA)
1						
2						
3						
4						
5						
6						
7						
8						

Graph is plotted on graph paper

 

Result: The drain and transfer characteristics of FET is observed and the plotted on graph paper.

AC drain resistance $r_d = \underline{\hspace{2cm}}$ ohm

Trans-conductance $g_m = \underline{\hspace{2cm}}$ mho

Amplification factor $\mu = \underline{\hspace{2cm}}$

Signature of Faculty

Date of Experiment _____

EXPERIMENT NO: 10

Aim: To plot the V-I Characteristics of Unijunction Transistor (UJT).

Apparatus Required:


1. Regulated Power Supply (0-30V, 1A) - 2Nos
2. UJT 2N2646
3. Resistors 100k Ω , 470k Ω
4. Voltmeter (0-30V) - 2no
5. Ammeter (0-30mA) - 1no.
6. Breadboard
7. Connecting Wires

Theory: A Unijunction Transistor (UJT) is an electronic semiconductor device that has only one junction. The UJT Unijunction Transistor (UJT) has three terminals an emitter (E) and two bases (B1 and B2). The base is formed by lightly doped n-type bar of silicon. Two ohmic contacts B1 and B2 are attached at its ends. The emitter is of p-type and it is heavily doped. The resistance between B1 and B2, when the emitter is open-circuit is called inter-base resistance. The original unijunction transistor, or UJT, is a simple device that is essentially a bar of N type semiconductor material into which P type material has been diffused somewhere along its length. The 2N2646 is the most commonly used version of the UJT.

The UJT is biased with a positive voltage between the two bases. This causes a potential drop along the length of the device. When the emitter voltage is driven approximately one diode voltage above the voltage at the point where the P diffusion (emitter) is, current will begin to flow from the emitter into the base region. Because the base region is very lightly doped, the additional current (actually charges in the base region) causes (conductivity modulation) which reduces the resistance of the portion of the base between the emitter junction and the B2 terminal. This reduction in resistance means that the emitter junction is more forward biased, and so even more current is injected.

Overall, the effect is a negative resistance at the emitter terminal. This is what makes the UJT useful, especially in simple oscillator circuits. When the emitter voltage reaches V_p , the current starts to increase and the emitter voltage starts to decrease. This is represented by negative slope of the characteristics which is referred to as the negative resistance region, beyond the valley point, R_{B1} reaches minimum value and this region, V_{EB} proportional to I_E .

Circuit Diagram:

 


Procedure:

1. Connect the circuit as shown in above figure.
2. Keep $V_{BB} = 5V$, Vary V_{EB} smoothly with fine control such that V_E Varies in steps of 0.5 volts from zero and note down the resulting emitter current I_E for each step in the tabular form.
3. Repeat the experiment for $V_{BB} = 7V$ and for $V_{BB} = 10V$.
4. Draw the graph between V_{EB} Vs I_E by keeping V_{BB} constant.

Observation:

Sr. No.	$V_{BB} = \underline{\hspace{1cm}}$ volts		$V_{BB} = \underline{\hspace{1cm}}$ volts		$V_{BB} = \underline{\hspace{1cm}}$ volts	
	V_{EB} (V)	I_E (mA)	V_{EB} (V)	I_E (mA)	V_{EB} (V)	I_E (mA)
1						
2						
3						
4						
5						
6						
7						
8						

Graph is plotted on graph paper

 

Result: The V-I Characteristics of UJT is plotted on graph paper.

Signature of Faculty